



KWAME NKRUMAH UNIVERSITY OF SCIENCE AND TECHNOLOGY

KUMASI, GHANA

COLLEGE OF ENGINEERING

DEPARTMENT OF COMPUTER ENGINEERING

COE 381: MICROPROCESSORS

MICROPROCESSOR CIRCUIT DESIGN

MAY 2022

GROUP ALTERA

| | Name | Index |
|----|--------------------------------------|---------|
| 1. | Sven Dzeble | 8258719 |
| 2. | Max Tetteh Otuteye | 8265019 |
| 3. | Prince Elikplim Kofi | 8251119 |
| 4. | Dillys Naa Kai Annan | 8253919 |
| 5. | Danso Eric Obeng Akese | 8257919 |
| 6. | Biritwum-Nyarko Kwasi Manu | 8257119 |
| 7. | Hansen Kwadwo Koduah Junior | 8260019 |
| 8. | Frank Kwamena Nana Edu Kotsia Appiah | 8254419 |

DECLARATION

We, the undersigned solemnly declare that the project report dubbed 'MICROPROCESSOR CIRCUIT DESIGN' is based on work conducted during study.

We assert the statements made and conclusions drawn are an outcome of our research work. We further certify that

- I. The work contained in the report is original and has been done by this team.
- II. The work has not been submitted to any other Institution for any other degree/certificate in this university or any other university.
- III. The guidelines provided by the university in authoring the report have been followed.
- IV. Whenever materials (data, theoretical analysis, and text) have been used from other sources, due credit to them in the text of the report and giving their details in the references have been given.

ABSTRACT

A microprocessor is a computer processor where the data processing logic and control is included on a single integrated circuit, or a small number of integrated circuits. The microprocessor contains the arithmetic, logic, and control circuitry required to perform the functions of a computer's central processing unit. "Altera" integrated this concept into designing a simple microprocessor that performs operation on operands to produce a desired output.

DEDICATION

We dedicate this project to God Almighty our creator, strong pillar, source of inspiration, wisdom, knowledge and understanding. He has been the source of our strength throughout this programme and on His wings only have we soared.

ACKNOWLEDGEMENTS

We would like to express our special thanks of gratitude to Mr. J. Yankey, our Microprocessors lecturer who gave us the excellent opportunity to work on this project, 'MICROPROCESSOR DESIGN CIRCUIT.' This project has helped learn and understand microprocessors better through research. We are very thankful. Secondly, we would like to thank each group member for their various contributions and commitment to making this project a success.


TABLE OF CONTENT

| DECLARATION | 02 |
|--|--|
| ABSTRACT | 03 |
| DEDCATION | 04 |
| ACKNOWLEDGEMENTS | 05 |
| TABLE OF CONTENT | 06 |
| INTRODUCTION | 07 |
| POWER SUPLLY CIRCUIT | 07 |
| FLAGS | 07 |
| CARRY FLAG | 08 |
| ZERO FLAG | 08 |
| NEGATIVE FLAG | 08 |
| REGISTERS | 09 |
| GENERAL PURPOSE REGISTERS | 09 |
| TEMPORARY ADDRESS REGISTERS | 10 |
| IMMEDIATE VALUE REGISTER | 10 |
| MEMORY ADDRESS REGISTER | 10 |
| MEMORY BIFFER REGISTER | 11 |
| RANDOM ACCESS MEMORY | 11 |
| REGISTER A DND B | 11 |
| PROGRAM COUNTER | 12 |
| ARITHMETIC AND LOGIC UNIT | 12 |
| CONTROL UNIT | 13 |
| ASSEMBLER | 17 |
| CONCLUSION | 17 |
| REFREMCES | 18 |
| DEVELOPERS | 18 |
| APPENDIX | 18 |
| LIST OF TABLES | |
| TABLE 1.0 | 0.7 |
| TABLE 2.0 | 07 |
| TABLE 2.0 | 0.7 |
| | 07 |
| LIST OF FIGURES | 07 |
| LIST OF FIGURES FIGURE 1.0 | 07 07 |
| | |
| FIGURE 1.0 | 07 |
| FIGURE 1.0 FIGURE 2.0 | 07 07 |
| FIGURE 2.0 FIGURE 2.1 | 07 07 08 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 | 07 07 08 08 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 | 07 07 08 08 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 FIGURE 3.0 | 07 07 08 08 08 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 FIGURE 3.0 FIGURE 3.1 | 07 07 08 08 08 09 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 FIGURE 3.0 FIGURE 3.1 FIGURE 3.1 | 07 07 08 08 08 09 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 FIGURE 3.0 FIGURE 3.1 FIGURE 3.2 FIGURE 3.3 | 07 07 08 08 08 09 09 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 FIGURE 3.0 FIGURE 3.1 FIGURE 3.2 FIGURE 3.3 FIGURE 3.3 | 07 07 08 08 08 09 09 10 10 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 FIGURE 3.0 FIGURE 3.1 FIGURE 3.2 FIGURE 3.3 FIGURE 3.4 FIGURE 3.5 | 07 07 08 08 08 09 09 10 10 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 FIGURE 3.0 FIGURE 3.1 FIGURE 3.2 FIGURE 3.3 FIGURE 3.5 FIGURE 4.0 | 07 07 08 08 08 09 09 10 10 11 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 FIGURE 3.0 FIGURE 3.1 FIGURE 3.2 FIGURE 3.3 FIGURE 3.5 FIGURE 5.0 | 07 07 08 08 08 09 09 10 10 11 |
| FIGURE 1.0 FIGURE 2.0 FIGURE 2.1 FIGURE 2.2 FIGURE 2.3 FIGURE 3.0 FIGURE 3.1 FIGURE 3.2 FIGURE 3.3 FIGURE 3.5 FIGURE 5.0 FIGURE 5.0 FIGURE 6.0 | 07 07 08 08 08 09 09 10 10 11 11 11 |

INTRODUCTION

NitroCompute is a 16-bit processor designed based on Vonn Neuman architecture. It consists of a power supply, an Algorithm and Logic Unit (ALU), Registers, a Control Unit and Status Flags. Components were designed modularly; only the Control Unit determines what should be done at what instance. NitroCompute helps to perform basic operations with corresponding opcodes, together forming an instruction set.

POWER SUPLLY CIRCUIT

 

The power supply consists of a SR-flip flop. This is to ensure that the circuit stays active even if Set and Reset is zero once Set has an initial one value. The circuit is powered down either when Set and Reset is zero, a halt instruction from the Control Unit or the power off button which toggles reset

| Set | Reset | Output |
|-----|-------|-----------|
| 0 | 0 | No change |
| 0 | 1 | Reset |
| 1 | 0 | Set |
| 1 | 1 | invalid |

Table 1.0

FLAGS

 


Figure 2.0

Flags are a modified kind of register that record the condition of a microprocessor's calculation. The status of each flag determines the microprocessor's next action, thus enabling it to make decisions.

The **Set flag** is connected to the **write enabled** which determines whether to set flag or not **Clock** determines when values are updated

| Parameter | Description |
|-----------|----------------|
| D | Data in |
| WE | Write Enabled |
| Q | Output |
| R | Reset (unused) |

Table 2.0

CARRY FLAG



Figure 2.1

The Carry Flag has a register to store the value of the flag. The Carry Flag in (CF_in) receives carry data and sends it to the register. Carry flag (CF) outputs flag state to the control unit.

ZERO FLAG

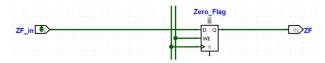


Figure 2.2

The **Zero Flag** has a register to store the value of the flag. The **Zero Flag in (ZF_in)** receives data and send to register. **Zero Flag(ZF)** outputs flag state to the control unit.

NEGATIVE FLAG

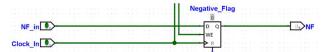


Figure 2.3

The **Negative Flag** has a register to store the value of the flag. The **Negative Flag in (NF_in)** receives data and send to register. **Negative Flag(ZF)** outputs flag state to the control unit.

REGISTERS

 


Figure 3.0

The temporary storage locations inside the Central processing Unit to store data and addresses is called a register.

GENERAL PURPOSE REGISTERS

 


Figure 3.1

The general-purpose register can store a data or a memory location address. It is a multipurpose register. They can be used either by programmer or by a user. For NitroCompute, Write Enabled (WE) determines whether to store or not from Data In (D_in). Output Enabled (OE) determines whether to output the content of selected register. Register Bank Select (Rb_sel) tunnel helps to select a register whose content should be displayed. The Demultiplexer helps to select a specific register based on rb_sel value. The Multiplexer is used in selecting data to be outputted. Register Bank Output Enabled (rb_OE) determines whether data stored in register should be outputted. Data out (D_out) is the data being outputted

TEMPORARY ADDRESS REGISTER

 


Figure 3.2

This **Address Register** was previously called the **Instruction Register**. It receives data from **the internal bars**. Based on the **bit select** value, either the first eight bits or second eight bits would be selected. It consists of a **latch** as well as **write and output enablers** to decide whether to write data or to output its result. It also consists of a **controlled buffer** which determines whether the output should be sent to the internal address bars.

IMMEDIATE VALUE REGISTER

 


Figure 3.3

The **immediate value register** stores the immediate value in every instruction (**first eight bits**). It receives input from instruction and outputs data to the internal data bars. It consists of a **bit extender** to push additional zeros to the instruction bits to enable data to be compatible with the number of bits received on the data bars.

MEMORY ADDRESS REGISTER

 


Figure 3.4

This register receives eight bits of data. It is **negatively clocked (enabled on falling edge)** to enable the program counter successfully to clock (**synchronization**). It also has a write enabler and output enabler to decide whether to write and store data values at each instance.

The memory address register pushes data to the external address bus (RAM).

MEMORY BIFFER REGISTER

 


Figure 3.5

The memory buffer register is a bridge between the internal and external data bars. (Two-way bridge). It can write to both the internal and external data bars as well as receive input from either data bars. It has an output enabler which determines whether data should be pushed out of this register.

RANDOM ACCESS MEMORY

 


Figure 4.0

The RAM has a total of 256 x 16 bits of data Its first 128 bits are for storing addresses and second 128, for data. It has a write enabler to determine whether data should be written to the RAM and an output enabler to determine whether data should be fed to the external data bars.

REGISTER A AND B

 


Figure 5.0

These are the only inputs to Arithmetic and Logic Unit. They serve as data input for ALU operations.

PROGRAM COUNTER

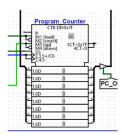


Figure 6.0

The program counter determines in what order instructions are fetched and executed. It can either load and count but not both at an instance and count upwards or and downwards. It also has a count enable as well as a reset. It has memory to store count values. It has an output enabler to decide whether to write to internal data bus. The Program Counter has max value 7f (hexadecimal) after which it restarts counting

ARITHMETIC AND LOGIC UNIT

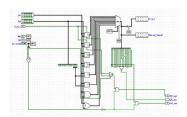


Figure 7.0

The Arithmetic and Logic Unit is a digital circuit used to perform arithmetic and logic operations. It represents the fundamental building block of the central processing unit.

The Instruction Format for an ALU is:

[OPCODE][SOURCE1][SOURCE2][DESTINATION]

Under this ALU, there are eight operations.

| • | • | 0 | - | ADD | - | ADDITION |
|---|---|---|---|------------|---|------------------------|
| • | • | 1 | - | SUB | - | SUBTRACTION |
| • | • | 2 | - | MULT | - | MULTIPLICATION |
| • | • | 3 | - | DIV | - | DIVISION |
| • | • | 4 | - | SHL | - | LOGICAL SHIFT LEFT |
| • | • | 5 | - | SHR | - | LOGICAL SHIFT RIGHT |
| • | • | 6 | - | AND | - | LOGICAL MULTIPLICATION |
| | | 7 | _ | Ω R | _ | LOGICAL ADDITION |

The ALU receives data from Register 1 and Register 2 (Register A and B). Every operation aside Logical Shift Left, and Logical Shift Right use 16-bit values. All eight operations are performed on the operands. A Multiplexer and Write Enabler (WE) determine which output should be displayed and whether an operation should be performed. Data Out (D_out) sends data to internal address bus. Stored_Result shows current result. The Negative Flag and Carry Flag are only triggered by the Add and Sub operations. If the result of the operation exceeds sixteen bits, the Carry Flag is triggered. The Negative flag is triggered when the Logical Union of the result is zero.

For the **logical shift left and logical shift**, the **first operand** is **sixteen bits** and second is a **4-bit value** (**LSB**). **The Operation Code** received from **CU** determines which operation output to be displayed. The **Output Enable (OE)** determines whether the result should be displayed.

CONTROL UNIT

 


Figure 8.0

The control unit is the core of the entire Central Processing Unit. Its main operation is to generate control signals throughout the CPU to control when certain operations are performed. This control unit has twenty-nine control signals from zero to twenty-eight. For every operation, it checks for the enabled control signals and generates a control sequence for it to be performed.

The twenty-nine control signals are:

| ALU_OPCODE | - | 0 |
|--|---|---|
| ALU_OPCODE | - | 1 |
| ALU_OPCODE | - | 2 |
| MEMORYADDRESSREGISTER_INTERNALBUS_WRITEENABLED | - | 3 |
| IMMEDIATEVALUEREGISTER_WRITEENABLED | - | 4 |
| IMMEDIATEVALUEREGISTER_OUTPUTENABLED | - | 5 |

| ALU_WRITEENABLED | - | 6 |
|---|---|----|
| ALU_OUTPUTENABLED | - | 7 |
| PC_LOAD | - | 8 |
| PC_COUNTENABLED | - | 9 |
| PC_OUTPUTENABLED | - | 10 |
| MEMORYADDRESSREGISTER_WRITEENABLED | - | 11 |
| MEMORYADDRESSREGISTER_OUTPUTENABLED | - | 12 |
| RAM_WRITEENABLED | - | 13 |
| RAM_OUTPUTENABLED | - | 14 |
| INSTRUCTIONREGISTER_WRITEENABLED | - | 15 |
| INSTRUCTIONREGISTER_OUTPUTENABLED | - | 16 |
| REGISTERA_WRITEENABLED | - | 17 |
| REGISTERB_WRITEENABLED | - | 18 |
| MEMORYBUFFERREGISTER_WRITEENABLED | - | 19 |
| MEMORYBUFFERREGISTER_OUTPUTENABLED | - | 20 |
| MEMORYBUFFERREGISTER_INTERNALBUSENABLED | - | 21 |
| SET FLAG | - | 22 |
| GENERALPURPOSEREGISTER_SELECT | - | 23 |
| GENERALPURPOSEREGISTER_SELECT | - | 24 |
| GENERALPURPOSEREGISTER_SELECT | - | 25 |
| GENERALPURPOSEREGISTER_SELECT | - | 26 |
| GENERALPURPOSEREGISTER_WRITEENABLED | - | 27 |
| GENERALPURPOSEREGISTER_OUTPUTENABLED | - | 28 |
| | | |

The Control Unit performs the following operations with the following selected signals.

MOVR

This operation allows us to move the contents from one register to another register.

The syntax for a MOVR operation is,

[MOVR] [RA],[RB]

Where:

MOVR is the operation being performed

RA is the SOURCE register

RB is the **DESTINATION** register

MOVR1 = 3,19,23,24,25,26

MOVR2 = 20,21,23,24,25,26,27

MOVI

This operation allows us to move an immediate value into a register The syntax for a MOVI operation is,

Where:

MOVI is the operation being performed RA is the DESTINATION register IMME is the immediate value

MOVI1 = 4

MOVI2 = 5,23,24,25,26,27

LOAD

This operation allows us to load contents in memory into a register The syntax for a MOVI operation is,

Where:

LOAD is the operation being performed **RA** is the **DESTINATION** register **ADDR** is the address location of the data in memory.

LOAD1 = 5,11,12,14,15,16,19 LOAD2 = 5,21,23,24,25,26,27

STORE

This operation allows us to store the data from a register into memory. The syntax for a STORE operation is,

Where:

STORE is the operation being performed RA field is the SOURCE register ADDR is the address location to store the value

STORE1= 5,11,15,16

STORE1* = 11,15,16,23,24,25,26,28

STORE2 = 3,11,16,23,24,25,26,28

STORE3 = 12,13,20

JMP

This operation allows us to jump to a specified instruction location in memory. The syntax for a JMP operation is,

[JMP] [ADDR]

Where:

JMP is the operation being performed ADDR is the address location of the instruction to jump to

$$JMP1 = 5,15,16$$

JMPZ

This operation allows us to jump to a specified instruction location in memory if the zero flag is enabled, The syntax for a JMPZ operation is,

Where:

JMPZ is the operation being performed ADDR is the address location of the instruction to jump to

$$JMPZ = 5,15,16$$

JMPN

This operation allows us to jump to a specified instruction location in memory if the negative flag is enabled. The syntax for a JMPN operation is,

Where:

JMPN is the operation being performed ADDR is the address location of the instruction to jump to

$$JMPN = 5,15,16$$

HALT

This opcode halts the microprocessor 0x5e00 is fed into the Multiplexer The syntax for a HALT operation is.

[HALT]

Where:

HALT is the operation being performed

ALU OPERATIONS

[OPCODE][SOURCE1][SOURCE2][DESTINATION]

ALU1 = 17,23,24,25,26,28

ALU2 = 3,18,23,24,24,25,26,28

ALU3 = 6,7,22,23,24,25,26,27

ASSEMBLER



Figure 9.0

The NitroCompute Assembler was built using Python programming language and converts Assembly Language into hexadecimal code fed into The NitroCompute microprocessor. When executed, an application console which has a menu bar, text area and title bar appears.

The menu bar contains the following drop-down menus.

- File
 - Open: Allow user to provide input from a text file
 - Exit: Close application
- Save
 - Save: Store the content in the text area into a specified file.
- Assemble
 - Assemble: Allow user to convert the assembly code into a hexadecimal code and store the output into a specified file.

The text area is a rectangular are with a white background where the user can type the assembly code.

CONCLUSION

In designing NitroCompute, efficiency and cost were considered. Although it is not an ideal microprocessor, it is a start-up to undergo reviews and performance improvements together with The NitroCompute Assembler.

REFRENCES

- KNUST logo by source, Fair use, https://en.wikipedia.org/w/index.php?curid=24888272
- Definition of Microprocessor, Microprocessor Wikipedia
- Definition of Registers, <u>www.educba.com/register-in-microprocessor/</u>

DEVELOPERS

maxotuteye (Max Otuteye) (github.com) hanskod (Hansen Koduah) (github.com) dzeble (github.com) Adaks (github.com) Dillys3567 (github.com)

APPENDIX

https://github.com/maxotuteye/nitro-compute.git

ADD - ADDITION

ADDR - ADDRESS LOCATION OF THE DATA IN MEMORY.

ALU - ARITHMETIC AND LOGIC UNIT
AND - LOGICAL MULTIPLICATION

CF_ in - CARRY FLAG IN D_out - DATA OUT DIV - DIVISION

HALT - STOP MICROPROCESSOR IMME - IMMEDIATE VALUE

JMP - EXECUTE FROM SPECIFIED LOCATION IN MEMORY

JMPN - EXECUTE FROM LOCATION IF NEGATIVE FLAG IS TRIGGERED

JMPZ - EXECUTE FROM SPECIFIED LOCATION IF ZERO FLAG IS TRIGGERED

LOAD - PUSH CONTENT IN MEMORY TO REGISTER MOVI - IMMEDIATE VALUE TO REGISTER MOVE

MOVR - REGISTER TO REGISTER MOVE

MULT - MULTIPLICATION NF_in - NEGATIVE FLAG IN

NOP - STOP MICROPROCESSOR (NO OPERATION)

OE - OUTPUT ENABLED
OR - LOGICAL ADDITION
R1 - REGISTER 1

R2 - REGISTER 2 R3 - REGISTER 3 RA - REGISTER A RB - REGISTER B

Rb OE - REGISTER BANK OUTPUT ENABLED

Rb sel - REGISTER BANK SELECT

RC - REGISTER C SHL - SHIFT LEFT SHR - SHIFT RIGHT

STORE - SAVE DATA FROM REGISTER TO MEMORY

SUB - SUBTRACTION
WE - WRITE ENABLED
ZF_in - ZERO FLAG IN